

DRAFT

The PTR175 derived from the AN/ARC-52

The PTR175 is a VHF/ UHF transceiver, developed by Plessey in the UK , based on the AN/ARC-52 in the early seventies.

There are several improvements:

- The channel distance is 50kHz
- 370 VHF channels were added to the 3500 UHF channels.

UHF: receive and transmit between 225 and 399.95 MHz, RF output level 20W.

VHF: receive and transmit between 117.5 and 135.95 MHz, RF output level 3W

The transceiver includes either a separate receiver on 243 MHz, the guard channel, or an fsk demodulator for data transmission.

The extra functionality was possible by the use of miniature valves and relays, and some transistors.

There are two versions:

PTR175 with a dynamotor for DC only power supply;


PTR175A with transformer based power supply for 115V-400Hz supply



External connection is with the same 42-way plug as the ARC52; cable looms, interconnecting box and control can be interchanged. Of course the special PTR175 features are not available when an ARC52 control is connected.

All modules look identical between the ARC52 and the PTR175. However, the inside of the RF amplifier module (1) and the relay module (9) are totally different.

Prefix	Module
1	Main Receiver (VHF/UHF) including the VHF final (3W)
2	Variable IF
3	Fixed IF
4	Audio Amplifier
5	Spectrum Generator
6	RF Power Amplifier
7	Modulator
8	Guard Receiver
9	Relay Unit (includes the VHF first LO and smaller relays)
10	Power Supply or Dynamotor
11	Rectifiers in case of ac powered version
12	Mechanical Tuning Unit
15	Chassis
19	Oscillator

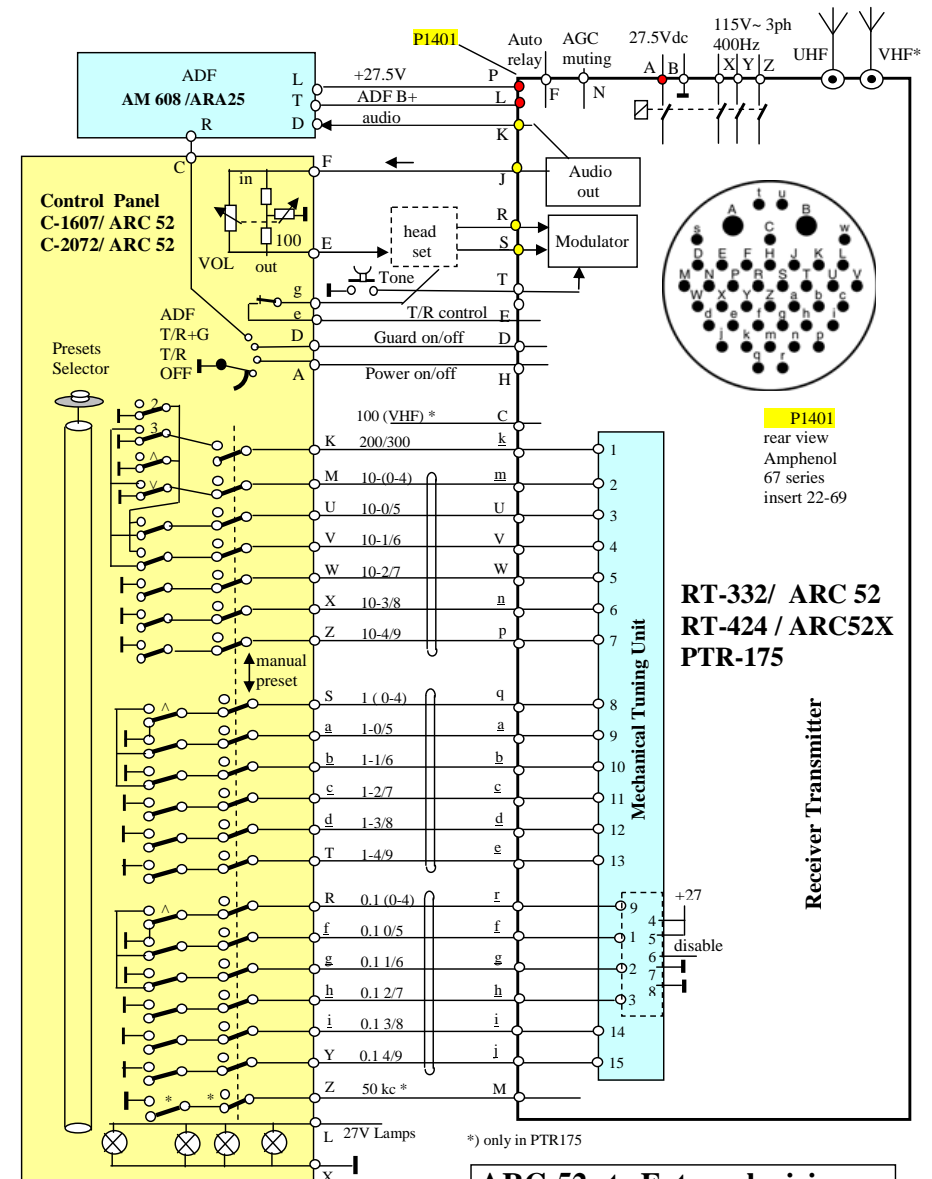Where the ARC52 receiver was a dual conversion superhet with 30 kHz bandwidth and 100kHz channel spacing, the PTR175 receiver is a triple conversion superhet with 20 kHz bandwidth and 50kHz channel spacing. The IF frequencies are 20-30MHz (tuned), 1.85MHz (fixed) and 500kHz (fixed, LC filters)




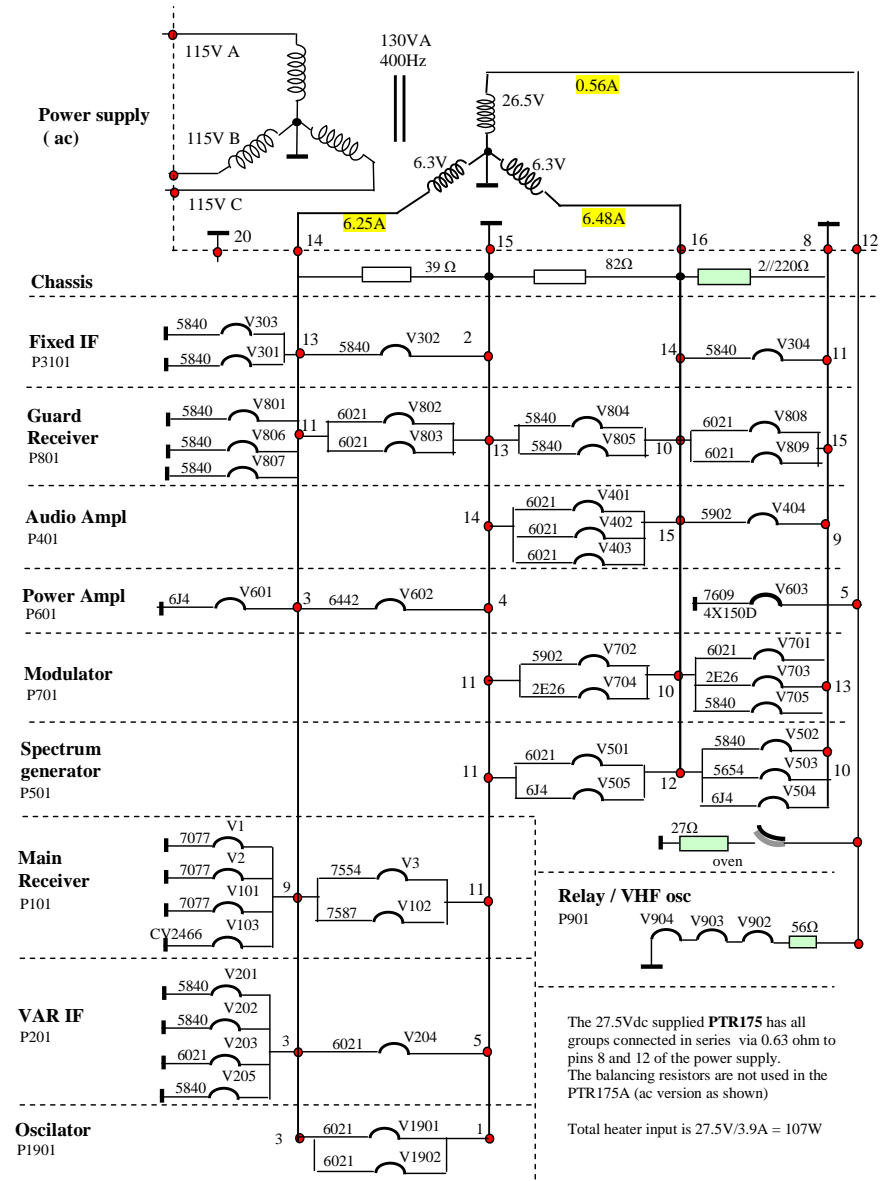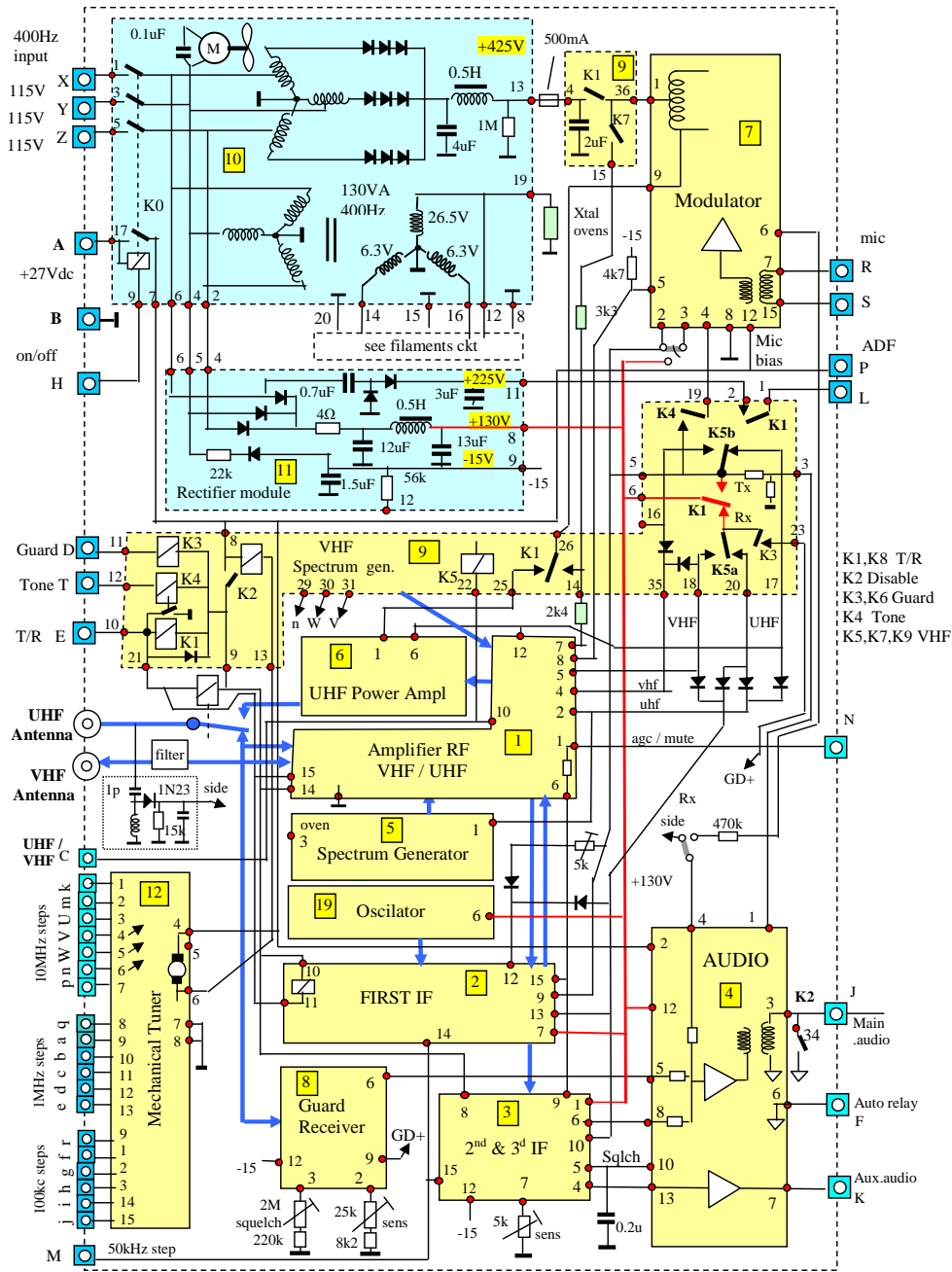


Coax Plug P 1401


PTR175A Main Chassis 12 May 2016

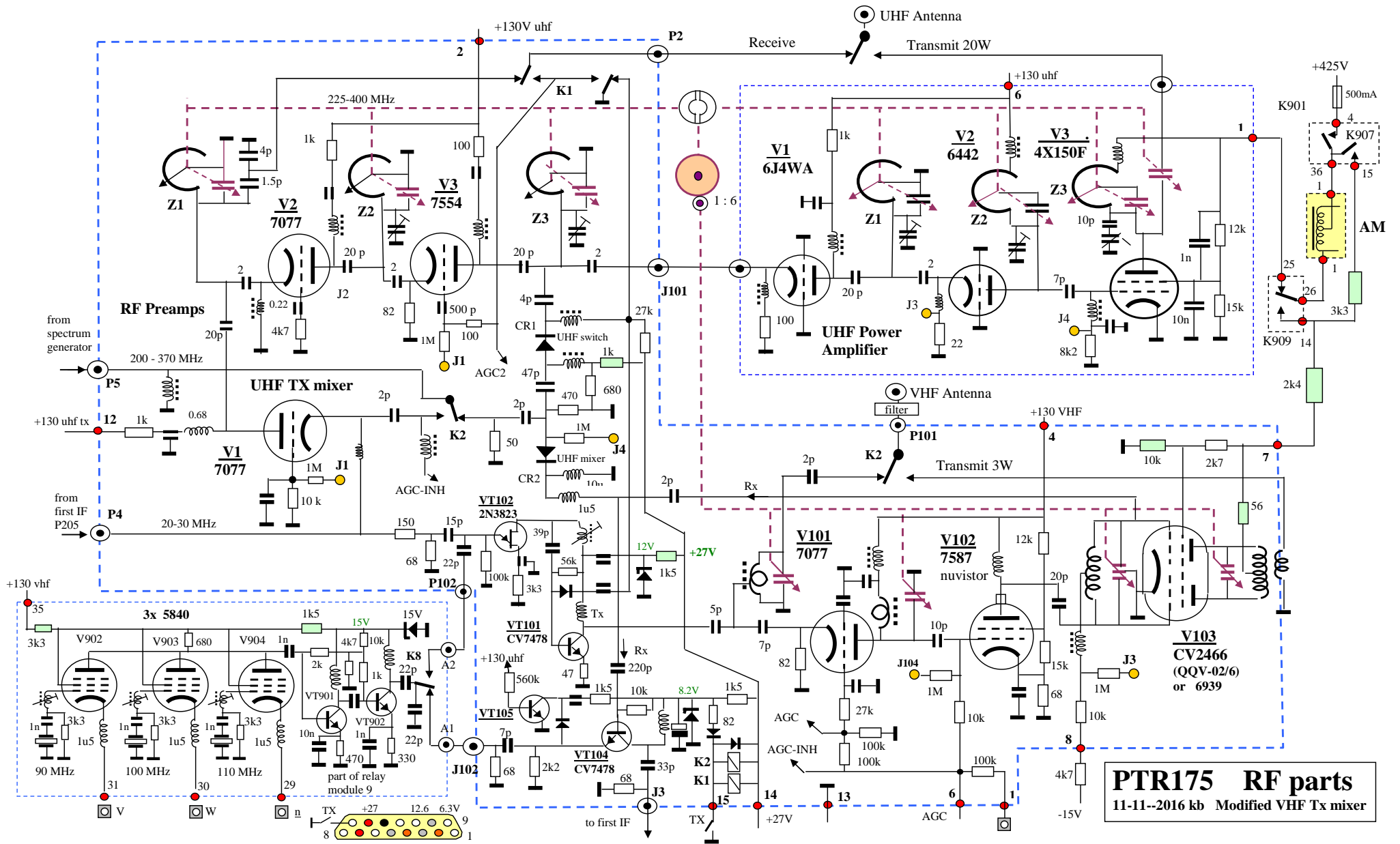PTR 175 and PTR175A Heater circuit
26 aug 2017 kb




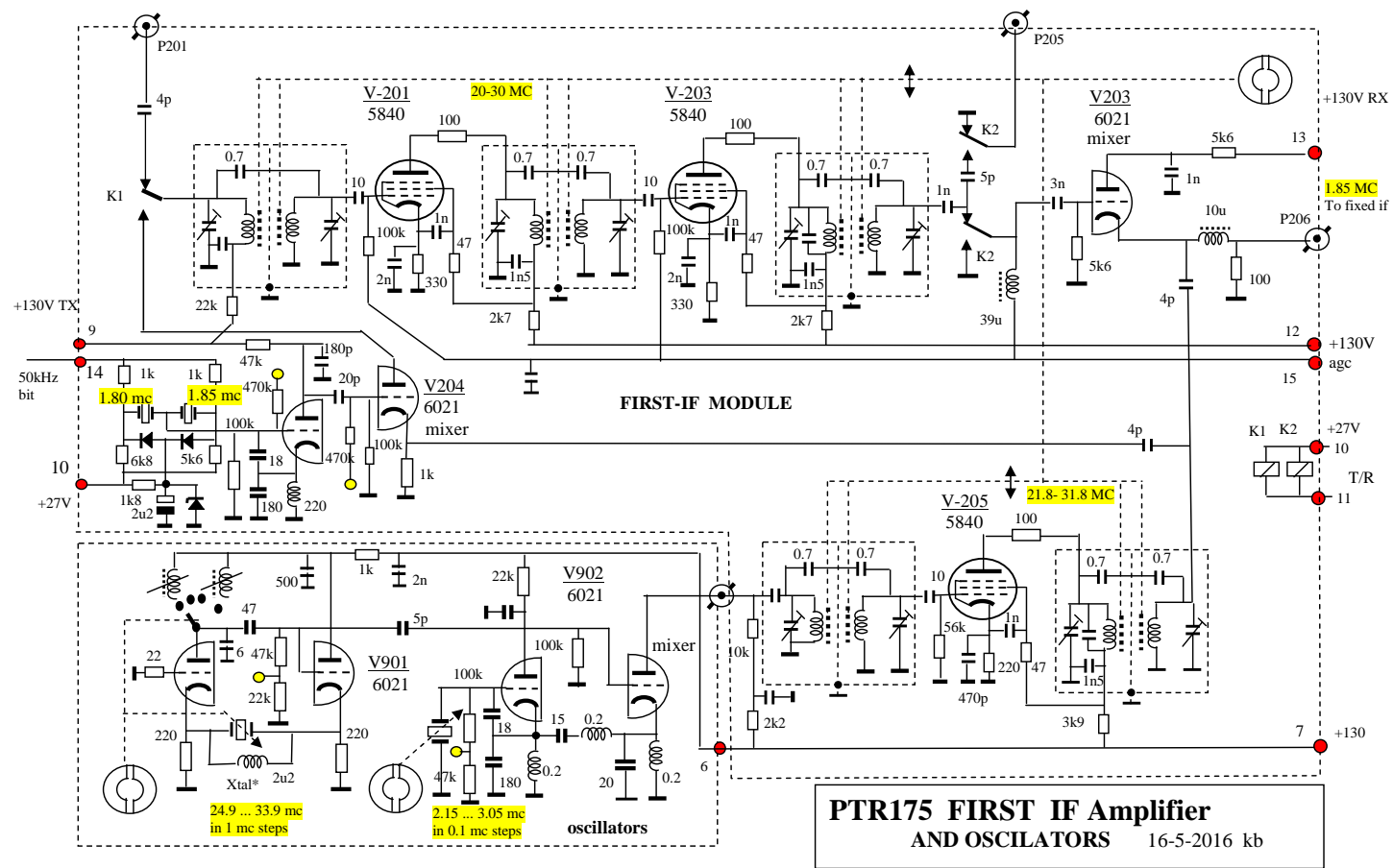PTR175 RF parts
 11-11--2016 kb Modified VHF Tx mixer



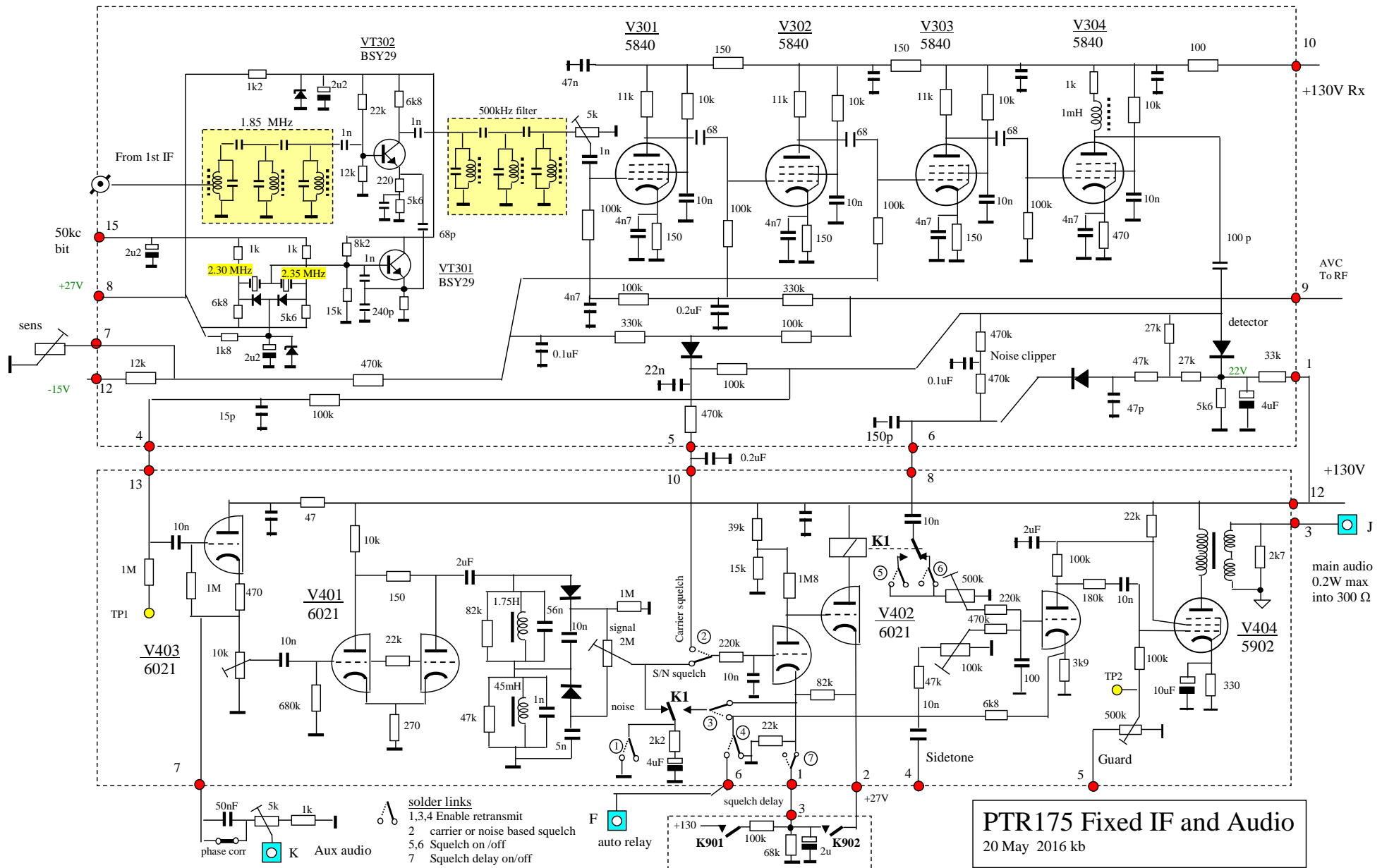

PTR175 Fixed IF and Audio
20 May 2016 kb

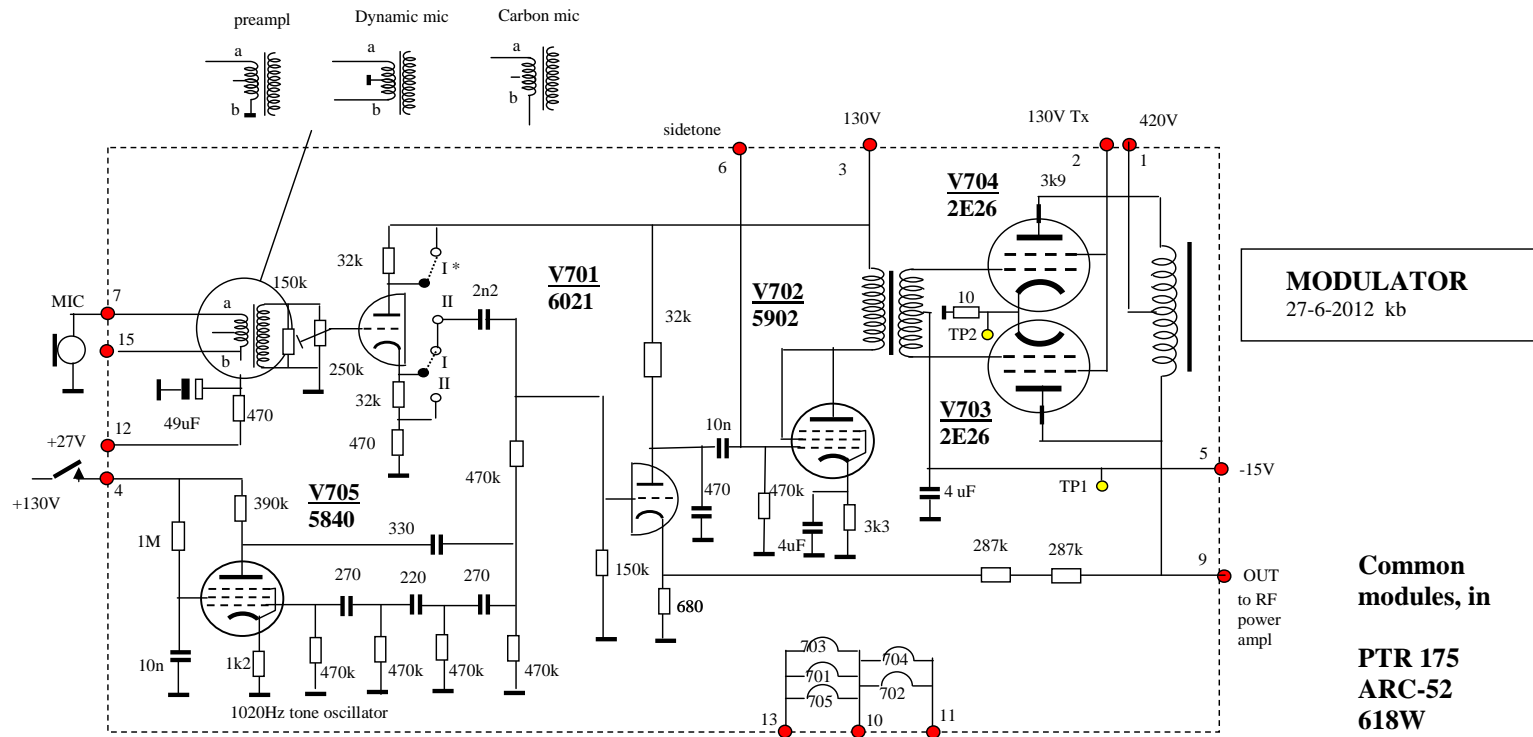

* Solderlinks I for use with preamplifier or carbon mike.
Solderlinks II for use with dynamic mike

First LO 200 - 370 MHz
in 18 steps of 10 MHz

5 Spectrum generator
(UHF first local oscillator)

Dial	Xtal	Mult	Freq
22	33.33	6	200
23	35.00	6	210
24	36.66	6	220
25	38.33	6	230
26	40.00	6	240
27	41.66	6	250
28	43.33	6	260
29	45.00	6	270
30	31.11	9	280
31	32.22	9	290
32	33.33 *	9	300
33	34.44	9	310
34	35.55	9	320
35	36.66*	9	330
36	37.77	9	340
37	38.88	9	350
38	40.00*	9	360
39	41.11	9	370

* Xtal dual used

